

ECE101-1L – FUNDAMENTALS OF ELECTRONIC CIRCUITS (LAB)

Activity #4 and 5: Transistor Familiarization and Application


Objectives:

- Use an Ohmmeter to differentiate between NPN and PNP transistors and to perform operational testing.
- Demonstrate the operation and biasing of a transistor under quiescent conditions.
- Demonstrate how to create and interpret transistor load lines.


Procedures:

1. Open Multisim
2. Create the circuit shown below

Diode Equivalent

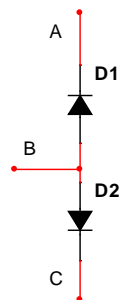

BJT NPN Transistor

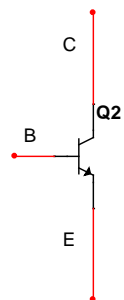


3. Using a multimeter (Ohmmeter Setting)
 - a. Connect the Multimeter Probe (+) to B terminal of Diode Equivalent Circuit and Probe (-) to A terminal. Screenshot the Multimeter Reading.
 - b. Connect the Multimeter Probe (+) to B terminal of BJT Transistor Circuit and Probe (-) to C terminal. Screenshot the Multimeter Reading.
 - c. Repeat the method used in a and b to complete the table:

Diode Equivalent Circuit		
Probe (+)	Probe (-)	Multimeter Reading
A	B	
B	C	
B	A	
C	B	

BJT NPN Transistor		
Probe (+)	Probe (-)	Multimeter Reading
B	C	
B	E	
C	B	
E	B	

- d. Base on the measurements above compare and discuss the operation of both circuit

4. Create the circuit shown below

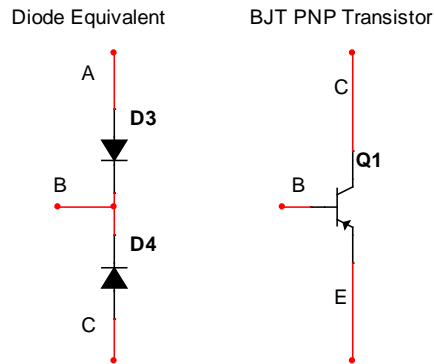

5. Using a multimeter (Ohmmeter Setting)
- Connect the Multimeter Probe (+) to B terminal of Diode Equivalent Circuit and Probe (-) to A terminal. Screenshot the Multimeter Reading.
-
- Connect the Multimeter Probe (+) to B terminal of BJT Transistor Circuit and Probe (-) to C terminal. Screenshot the Multimeter Reading.
-


- c. Repeat the method used in a and b to complete the table:

Diode Equivalent Circuit		
Probe (+)	Probe (-)	Multimeter Reading
A	B	
B	C	
B	A	
C	B	

BJT PNP Transistor		
Probe (+)	Probe (-)	Multimeter Reading
B	C	
B	E	
C	B	
E	B	

- d. Base on the measurements above compare and discuss the operation of both circuit
-
-

6. Create the circuit shown below

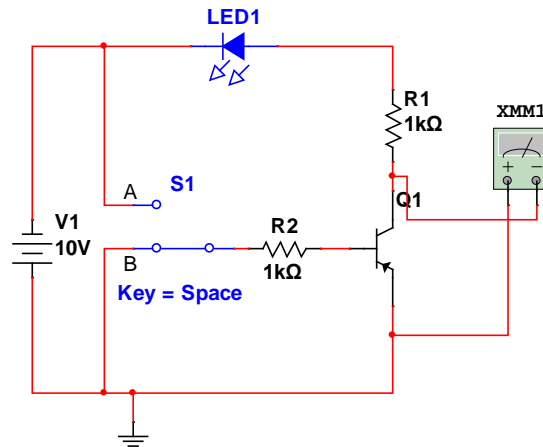


7. Run the Simulation, set the multimeter to Voltmeter settings

- At S1 at B position what is the Voltage reading in the multimeter
- By checking the voltage reading and the LED status. Is the circuit conducting or is there a current flowing through the LED?
- Set S1 at A position what is the Voltage reading in the multimeter
- By checking the voltage reading and the LED status. Is the circuit conducting or is there a current flowing through the LED?

8. Create the circuit shown below

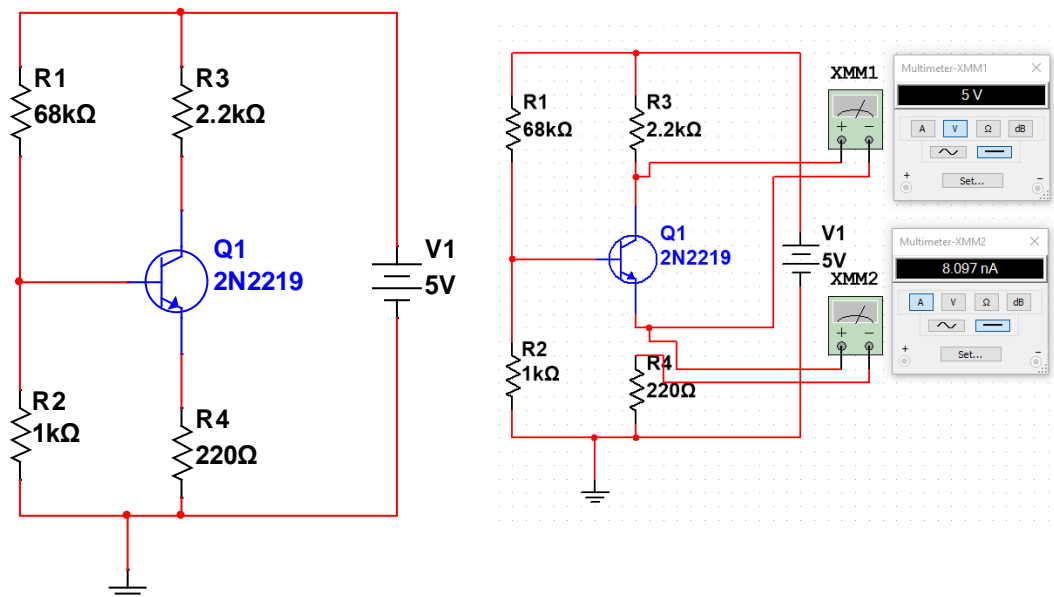9. Place a Multimeter to Measure the

- Voltage Across the Transistor (VCE) and
- Current flowing through the emitter (Ie)




10. Change the Value of R_2 and complete the table shown below.

$R_2(K\Omega)$	V_{CE}	I_E
1		
2		
5		
8		
15		
18		
20		
25		
30		

11. Use MSEXCEL or any spreadsheet software to graph the points (Scatter Plots)
 V_{CE} at horizontal axis and I_E at vertical axis

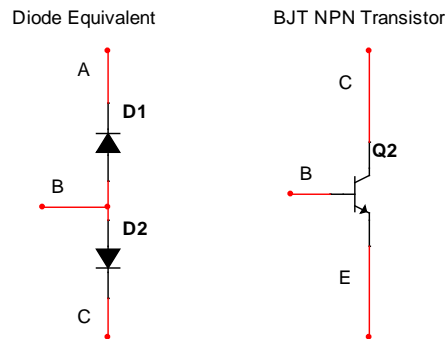12. Using TinkerCAD
13. Create the circuit shown below



14. Using a multimeter (Ohmmeter Setting)
 - a. Connect the Multimeter Probe (+) to B terminal of Diode Equivalent Circuit and Probe (-) to A terminal. Screenshot the Multimeter Reading.

 - b. Connect the Multimeter Probe (+) to B terminal of BJT Transistor Circuit and Probe (-) to C terminal. Screenshot the Multimeter Reading.

- c. Repeat the method used in a and b to complete the table:


Diode Equivalent Circuit		
Probe (+)	Probe (-)	Multimeter Reading
A	B	
B	C	
B	A	
C	B	

BJT NPN Transistor		
Probe (+)	Probe (-)	Multimeter Reading
B	C	
B	E	
C	B	
E	B	

- d. Base on the measurements above compare and discuss the operation of both circuit

- e. Does your TinkerCAD and Multisim simulation generate similar results?

15. Create the circuit shown below

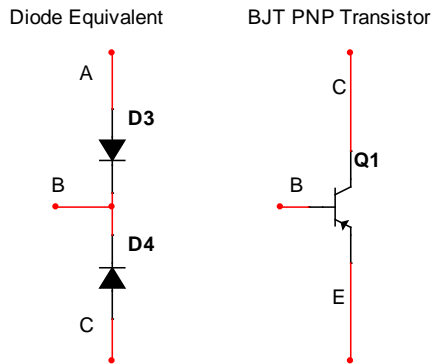

16. Using a multimeter (Ohmmeter Setting)

- Connect the Multimeter Probe (+) to B terminal of Diode Equivalent Circuit and Probe (-) to A terminal. Screenshot the Multimeter Reading.

- Connect the Multimeter Probe (+) to B terminal of BJT Transistor Circuit and Probe (-) to C terminal. Screenshot the Multimeter Reading.

c. Repeat the method used in a and b to complete the table:

Diode Equivalent Circuit		
Probe (+)	Probe (-)	Multimeter Reading
A	B	
B	C	
B	A	
C	B	

BJT PNP Transistor		
Probe (+)	Probe (-)	Multimeter Reading
B	C	
B	E	
C	B	
E	B	

d. Base on the measurements above compare and discuss the operation of both circuit

e. Does your TinkerCAD and Multisim simulation generate similar results?

Discussions:
